

Exam 2 Practice Test ANSWERS

1. B

2. B

Change in potential as we complete a loop must be zero. Starting from the point "b" and proceeding counter clockwise:

$$\Delta V = 16 - I(1.6) - I(5.0) - I(1.4) - 8 - I(9)$$

$$= 8 - I(1.6 + 5.0 + 1.4 + 9)$$

$$= 8 - I(17) \quad \therefore = 0$$

↑ Kirchhoff's Loop Rule

$$\therefore I = \frac{8}{17}$$

$$= 0.47 \text{ Amps}$$

3. D

4. A

$$I_1 R_1 = I_2 R_2 \quad (\text{Voltage drop from B to C is same for both paths})$$

$$I = I_1 + I_2 \quad \text{Kirchhoff's Junction Rule applied to junction B.}$$

use those 2 equations to solve for I_1 . 1st eq $\Rightarrow I_2 = I_1 \frac{R_1}{R_2}$

$$I = I_1 + I_1 \frac{R_1}{R_2} = I_1 \left(1 + \frac{R_1}{R_2}\right)$$

$$I_1 = \frac{I}{1 + \frac{R_1}{R_2}} = \frac{I R_2}{R_2 + R_1}$$

- 5 B
- 6 D
- 7 D
8. A
9. B
10. B
11. C
- 12 C
- 13 D
- 14 B
- 15 D
- 16 D
- 17 A
- 18 B
- 19 C
- 20 B
- 21 A
- 22 D
- 23 B
- 24 B
- 25 A
- 26 A
- 27 D
- 28 C
- 29 B
30. E