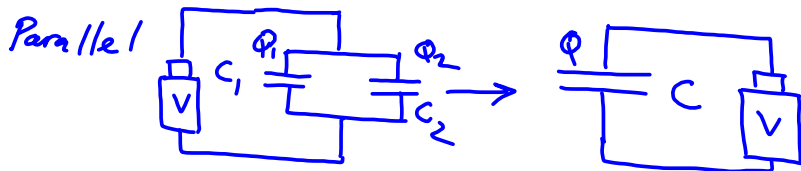


$$C = \frac{Q}{V} \quad C_1 = \frac{Q_1}{V_1} \quad C_2 = \frac{Q_2}{V_2}$$

$$C = \frac{Q}{V_1 + V_2} = \frac{Q}{\frac{Q}{C_1} + \frac{Q}{C_2}} = \frac{Q}{\frac{Q}{C_1} + \frac{Q}{C_2}}$$

$$= \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \rightarrow \boxed{\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}} \text{ Series}$$



$$C = \frac{Q}{V}$$

$$V = \frac{Q_1}{C_1} \quad V = \frac{Q_2}{C_2}$$


$$C_1 = \frac{Q_1}{V} \quad C_2 = \frac{Q_2}{V}$$

$$Q_1 + Q_2 = Q$$

$$C = \frac{Q_1 + Q_2}{V} = \frac{Q_1}{V} + \frac{Q_2}{V}$$

$$= C_1 + C_2$$

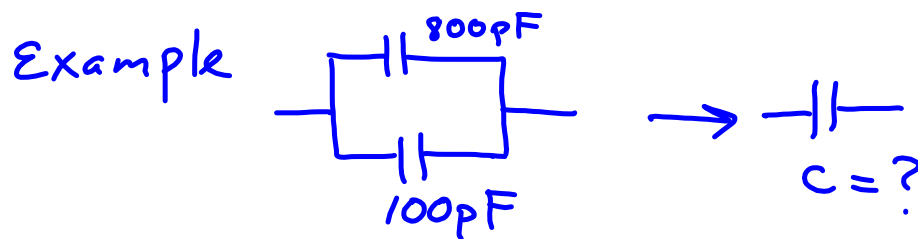
$$\boxed{C = C_1 + C_2} \text{ parallel}$$



$$C = C_1 + C_2$$

$$= 800 + 100 = 900\text{ pF}$$

↑ pico Farads
 $= 10^{-12}$ Farads

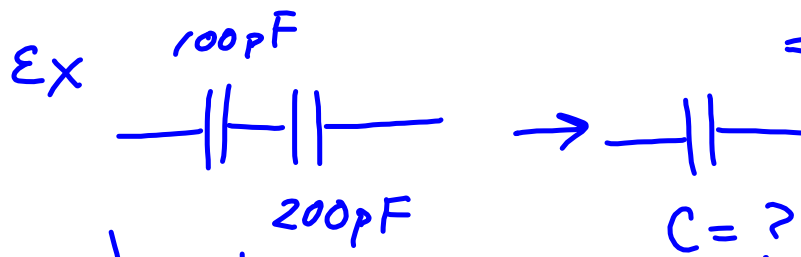


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$= \frac{1}{100} + \frac{1}{200} = \frac{2}{200} + \frac{1}{200} = \frac{3}{200}$$

$$C = \frac{200}{3} = 66.7\text{ pF}$$

Field Between Parallel Plate Capacitors

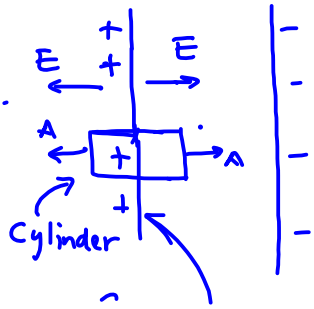

Gauss' Law

$$\left(\begin{array}{l} \text{electric} \\ \text{flux} \\ \text{thru surface} \end{array} \right) = 4\pi k Q_{\text{enclosed}}$$

$$\sigma = \frac{\text{charge}}{\text{area}}$$

$$(-E)(-A) + EA$$

$$2EA = 4\pi k A \sigma \quad A\sigma = Q$$

$$\bar{E} = 2\pi k \sigma$$



$$V = Ed$$

$$W = F \cdot d$$

$$\frac{W}{q} = \frac{F}{q} d$$

$$V = Ed$$

$$C = \frac{Q}{V}$$

$$= \frac{\sigma A}{E \cdot d} = \frac{\sigma A}{2\pi k \sigma d} = \frac{A}{2\pi k d}$$

$$C = \frac{1}{2\pi k} \frac{A}{d}$$

$$C = \frac{1}{4\pi k} \frac{A}{d}$$

because $\bar{E} = E_+ + E_- = 2\bar{E}$

↑
due to
+ plate


↑
due to
- plate

Capacitance of a
Parallel plate capacitor

Ex Parallel plate capacitor #1 2cm

" " " " #2 Same separation between plates.

How does C_2 compare to C_1 ?

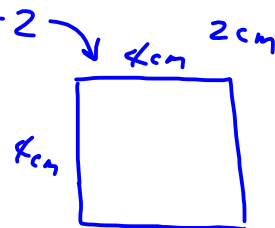


A. $C = \frac{1}{4\pi k} \frac{A}{d}$

$$C_1 = \frac{1}{4\pi k} \frac{2^2}{d} \propto 4$$

$$C_2 = 4C_1$$

$$C_2 = \frac{1}{4\pi k} \frac{4^2}{d} \propto 16$$

Dielectrics

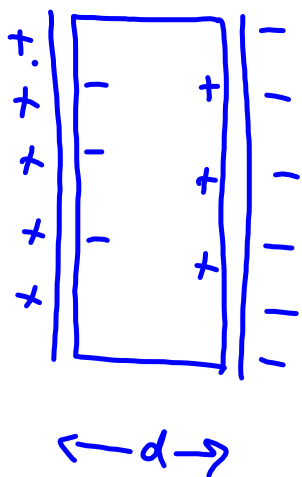

$$C = \frac{Q}{V}$$

If material has dielectric constant K , $V \rightarrow \frac{V}{K}$

$$C \rightarrow K C$$

$$E = \frac{V}{d} \Rightarrow E \rightarrow \frac{E}{K}$$