

11. $\phi = \frac{kq}{r} = V$ EXAM 1
Post mortem
 $\phi' = \frac{kq}{2r} = V/2$


5. $F = \frac{kq_1q_2}{r^2}$
 $r \rightarrow \leftarrow D-x \rightarrow$
 $\leftarrow D \rightarrow$

6. $\oplus \longleftrightarrow \oplus$ $E = \frac{-kq}{(D-x)^2} + \frac{kq}{x^2}$
 7. $E = \frac{kq}{r^2}$ $\phi = 2e$
 \uparrow
 $= 0 \text{ at } x = D/2$

8. $(-) \longleftrightarrow (+)$

10. $\leftarrow E$
 $\frac{W}{q} = \frac{F \cdot s}{q}$
 $V = E \cdot s$

 $\leftarrow s \rightarrow$

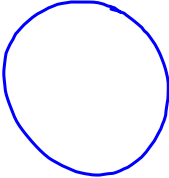12. 
 $\text{change in pot'l on equipotential surface} = 0$
 $\frac{W}{q} = \frac{F \cdot s}{q}$

13. $V \left\{ \begin{array}{l} \uparrow 0.1m \\ \downarrow \end{array} \right.$
 $V = E \cdot s$
 $E = \frac{V}{s} = \frac{12V}{0.1m} = 120 \frac{V}{m}$

$$14. C = \frac{Q}{V} \quad C_A = \frac{50C}{25V} = 2F$$

$$\rightarrow C_B = \frac{5C}{0.1V} = 50F$$

$$C_B > C_A$$

$$15. C = \epsilon_0 \frac{A}{d} = 8.85 \times 10^{-12} \frac{(1m)}{0.01}$$

$$= 8.85 \times 10^{-10} F$$

$$16. \frac{1}{C_B} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_B = \frac{1}{3}$$

$$= \frac{1}{1} + \frac{1}{.5} = 3$$

$$17. C_{eq} = C_1 + C_2$$

$$= 1 + 0.5 = 1.5F$$

$$18. E = \frac{1}{2} CV^2$$

$$E' = \frac{1}{2} C (2V)^2 = \frac{1}{2} C \cdot 4V^2 = 4E$$

$$= 4(4J) = \underline{\underline{16J}}$$

$$19. u = \frac{1}{2} \epsilon_0 E^2$$

$$E = \sqrt{\frac{2u}{\epsilon_0}} = \sqrt{\frac{2(.01J/m^3)}{8.85 \times 10^{-12} C^2/Nm^2}}$$


$$= \sqrt{2.26 \times 10^{10}}$$

$$= \sqrt{.24 \times 10^{10}}$$

$$= \sqrt{24 \times 10^8} =$$

$$= 4.8 \times 10^4 N/C$$

20.

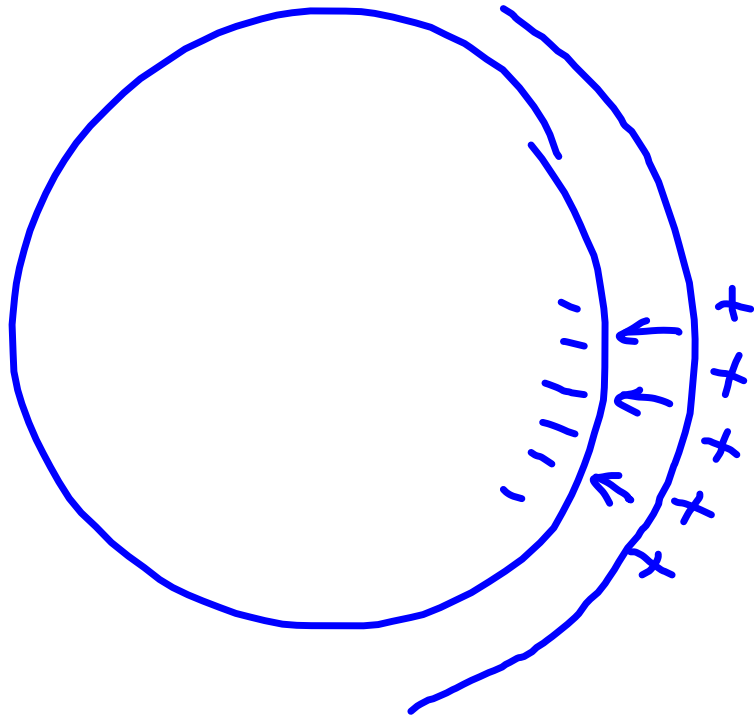

D.C. Circuits


Current = $\frac{\text{charge that flows past}}{\text{time required to flow past}}$
 $= \frac{\Delta q}{\Delta t}$

current is defined as the flow of positive charge (even though charges flowing in conductors are negative)



Unit of current = Ampere = $\frac{1 \text{ Coulomb}}{\text{Sec}}$

Symbol of current: I

Resistance


 $I = \frac{1}{R}V = \frac{V}{R}$ $I = \frac{V}{R}$ Ohm's Law

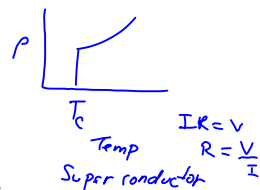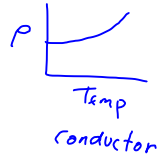$R = \rho \frac{L}{A}$ $\rho = \text{resistivity}$ ("like tree density")




$IR = V$
 $R = \frac{V}{I}$

Units of resistance = Ohm = $\frac{1 \text{ Volt}}{\text{Ampere}}$


Circuit symbol for resistor: 

Resistors in series

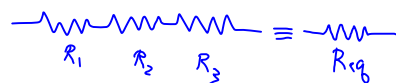

$R_{eq} = R_1 + R_2 + R_3$

Resistors in Parallel

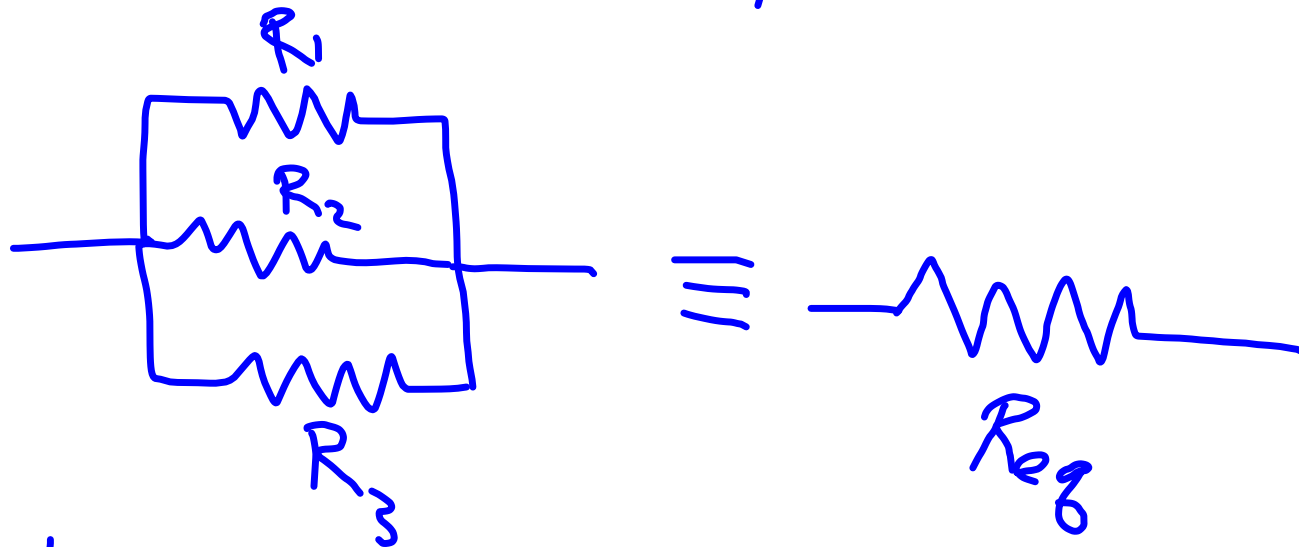

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$