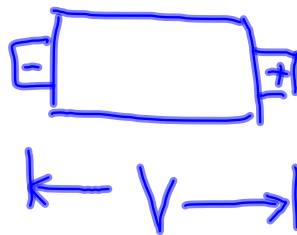


Electro motive Force (\mathcal{E} MF)

\mathcal{E} MF = potential difference between terminals of a battery with zero internal resistance

$$V = \mathcal{E} - Ir$$

small
resistance



\mathcal{E} MF is not a force

\mathcal{E} MF units are Volts

Power in a circuit

$$P = \frac{\Delta W}{\Delta t} = \frac{F \cdot s}{\Delta t}$$

$$= \frac{\frac{F}{\Delta q} \Delta q s}{\Delta t} = E \cdot s \frac{\Delta q}{\Delta t}$$


$$= E \cdot s \cdot I$$

$$= V I$$

$$P = IV$$

$$V = IR$$



$$P = \frac{V}{R} V = \frac{V^2}{R}$$

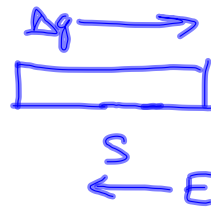

Kirchhoff's Rules


① Junction Rule

$$I_1 + I_2 + I_3 = 0$$

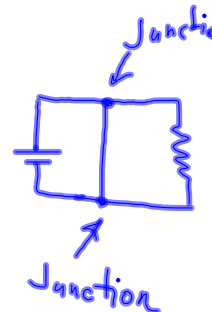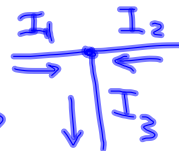

② Loop Rule



$$I_1 + I_2 = I_3$$

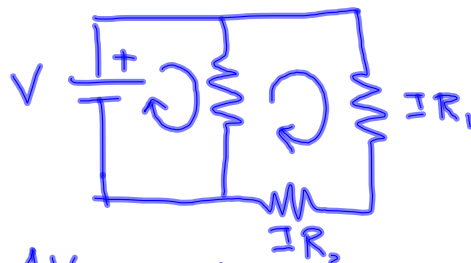

ΔV around any circuit loop = 0

$$V - IR_1 - IR_2 = 0$$

R-C Circuit

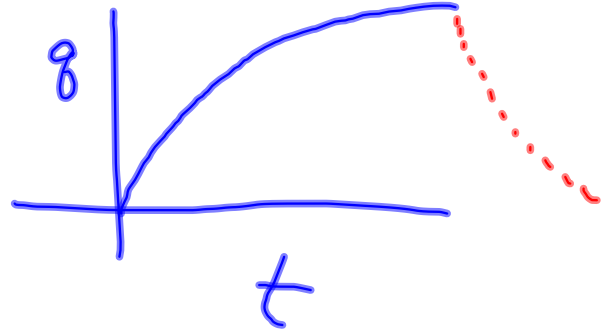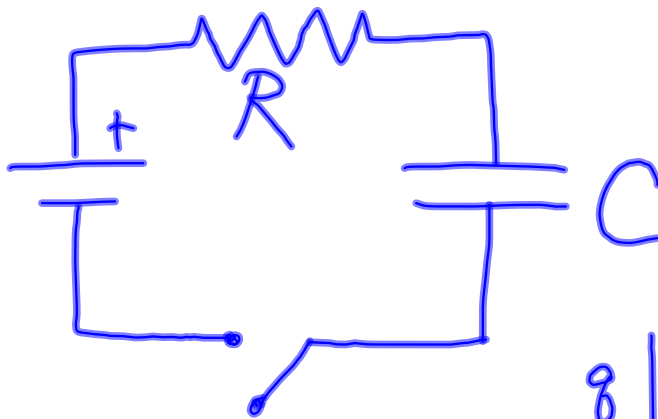

Time to charge or
discharge the capacitor
 $= RC$